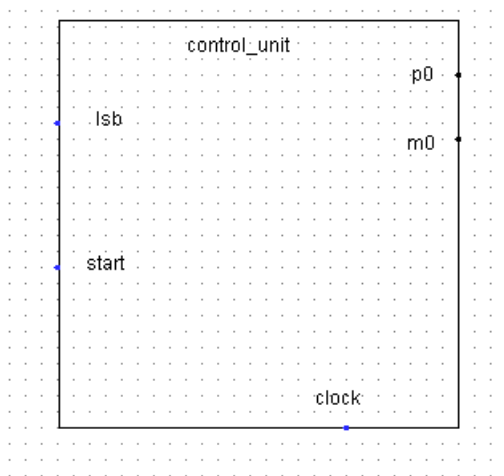


CSE 331/503
Computer Organization
Homework 3

Erkan Yilmaz
161044044

Components


Control_unit:




It has 2 output that have 2 bit p0 and m0 for choose operations on datapath

It has 2 input for choosing state

DFA for Control_unit

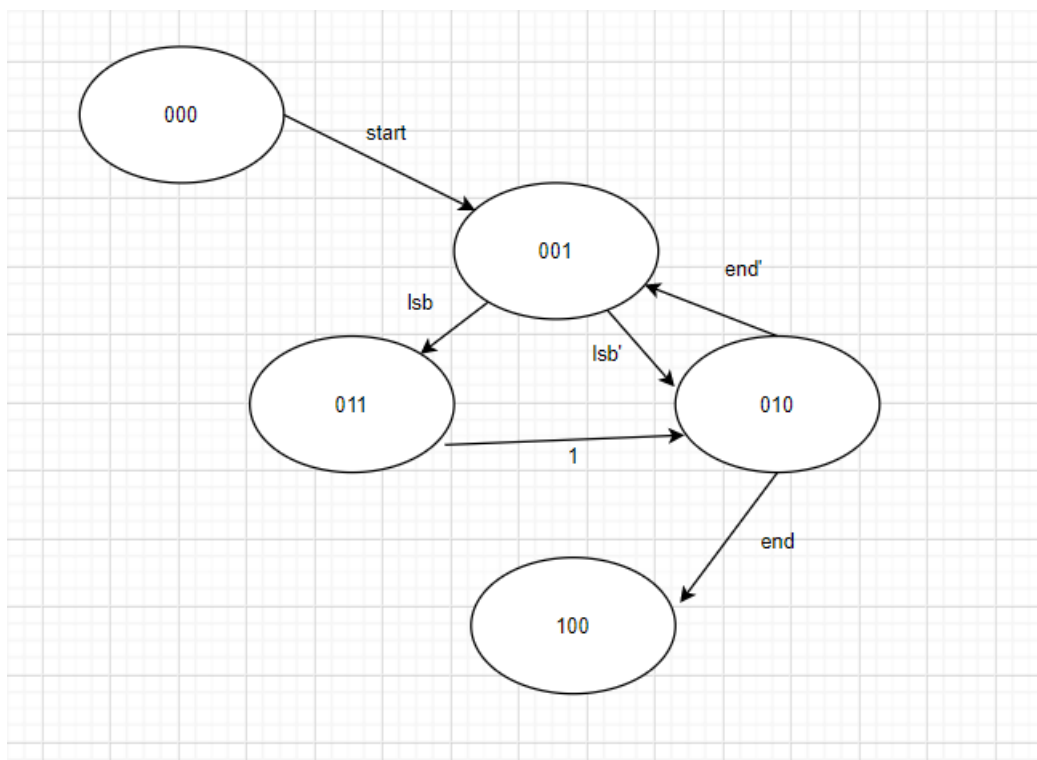

Datapath

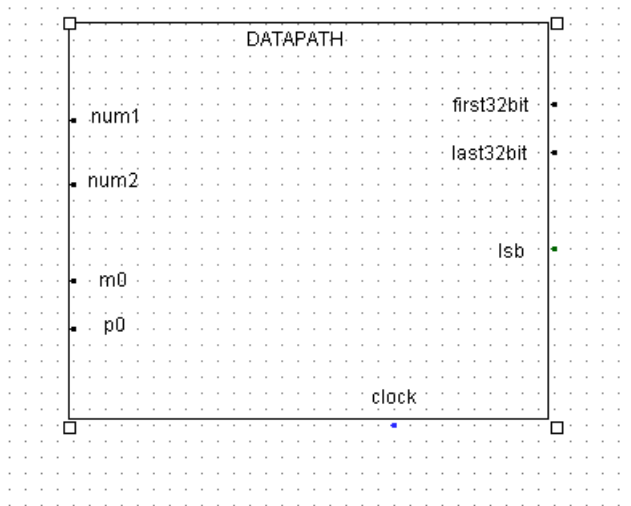

It has for input for choose operations on datapath


Num1 and num2 is numbers that we multiply

It has 3 output

Lsb for for choosing state of control unit

Other 2 outputs are result

64 bit shifter

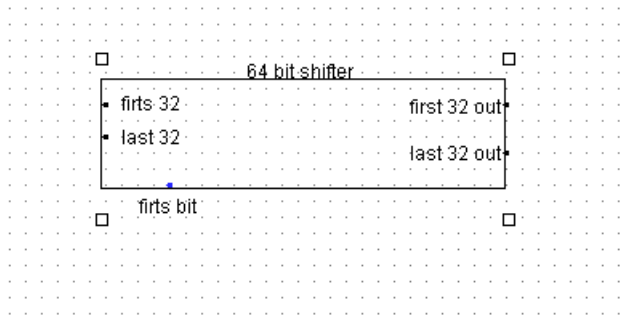


It has 2 inputs that are 32 bit and input is 1 bit

First 32 bit is first part of 64 bit number

Last 32 bit is last part of 64 bit number


First bit input is first bit of output you can choose is arithmetic or logical shift with using this bit

Check_end

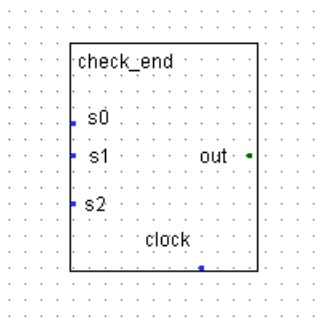


It is a circuit in control unit it gets state of control unit and says it is end of operations or not

Choose

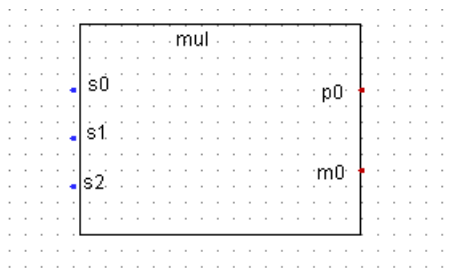


It is a circuit in control unit it get state of control unit and choose what operations will do on datapath

getLSB

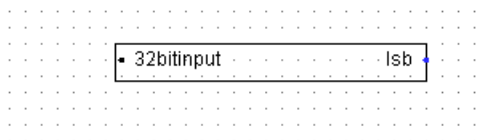


It has 32 bit 1 input and return less significant bit of it


Control Unit

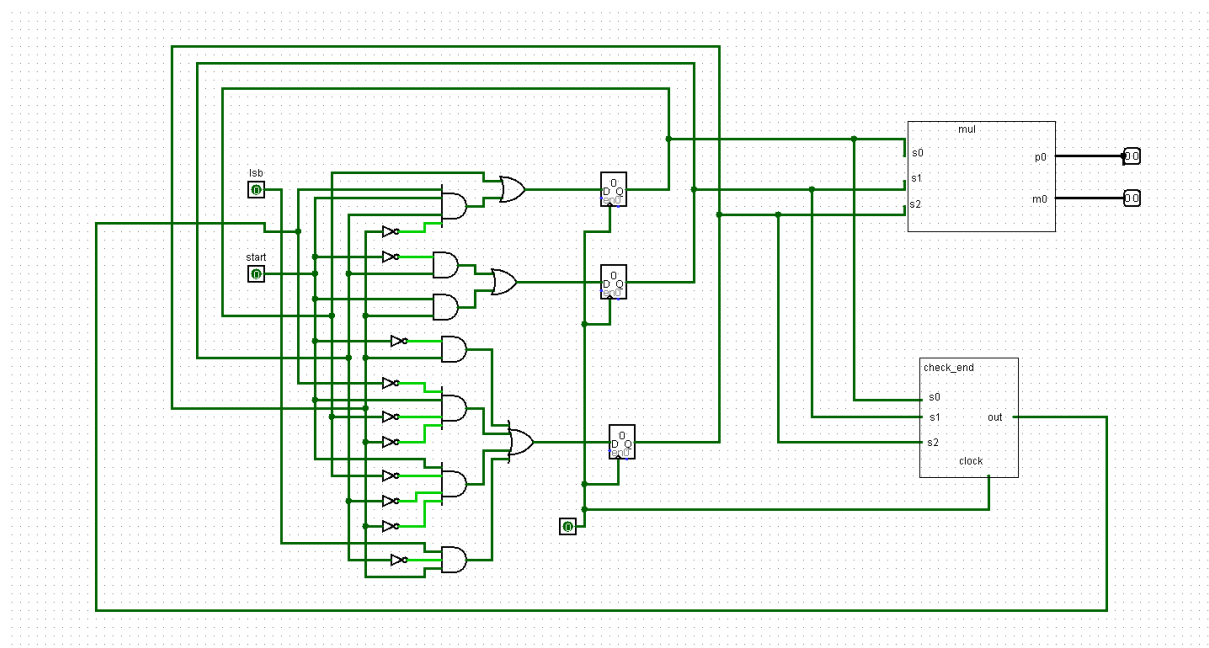


Datapath

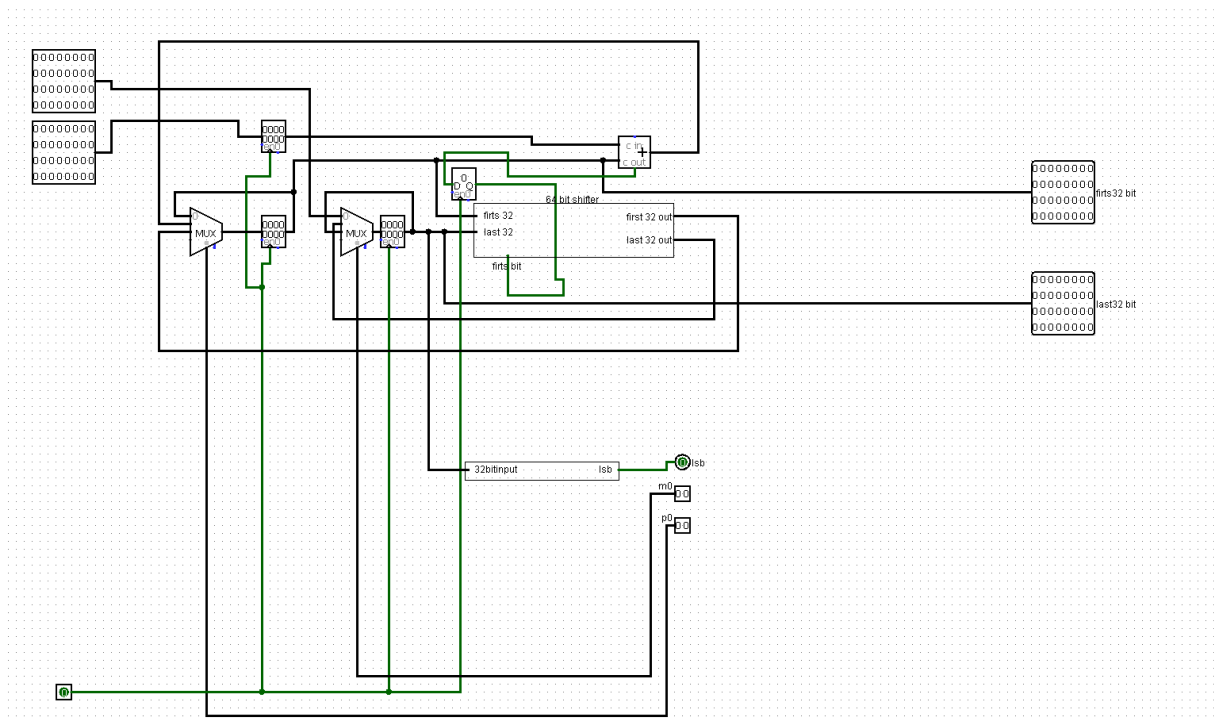


Test Case Result:

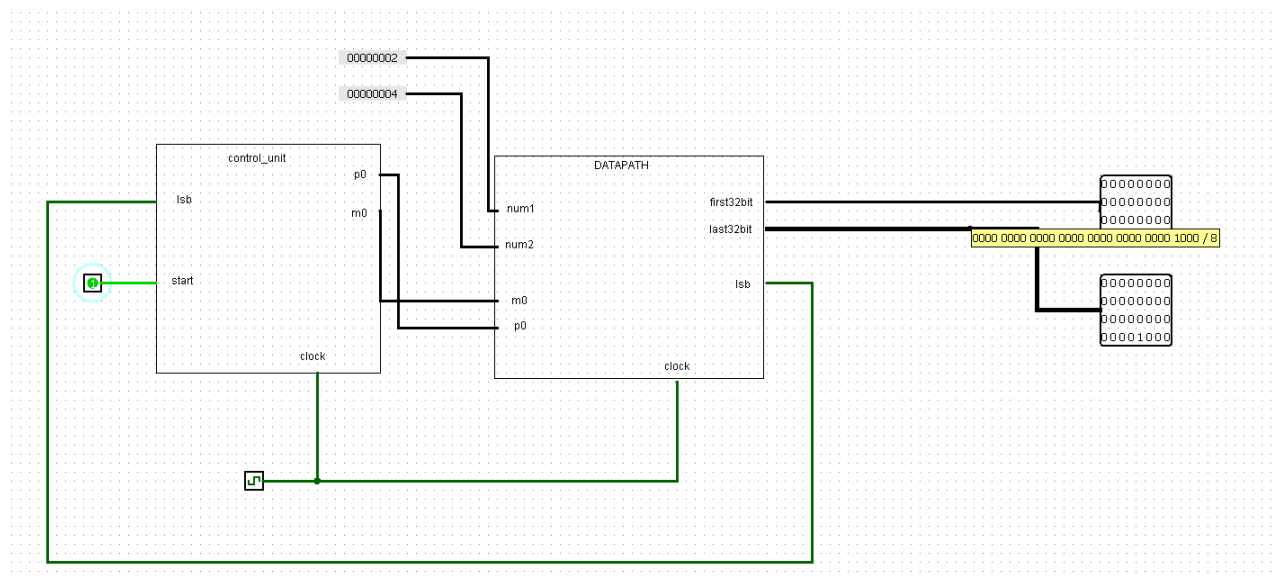


It Shows us $4 \times 2 = 8$

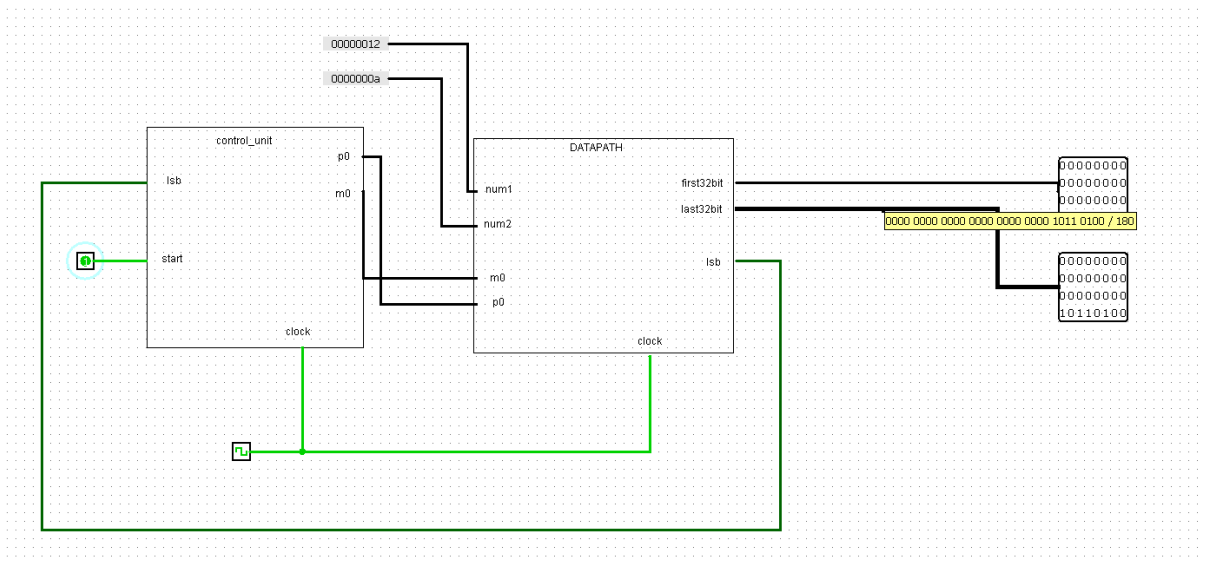


It shows us $18 * 10 = 180$

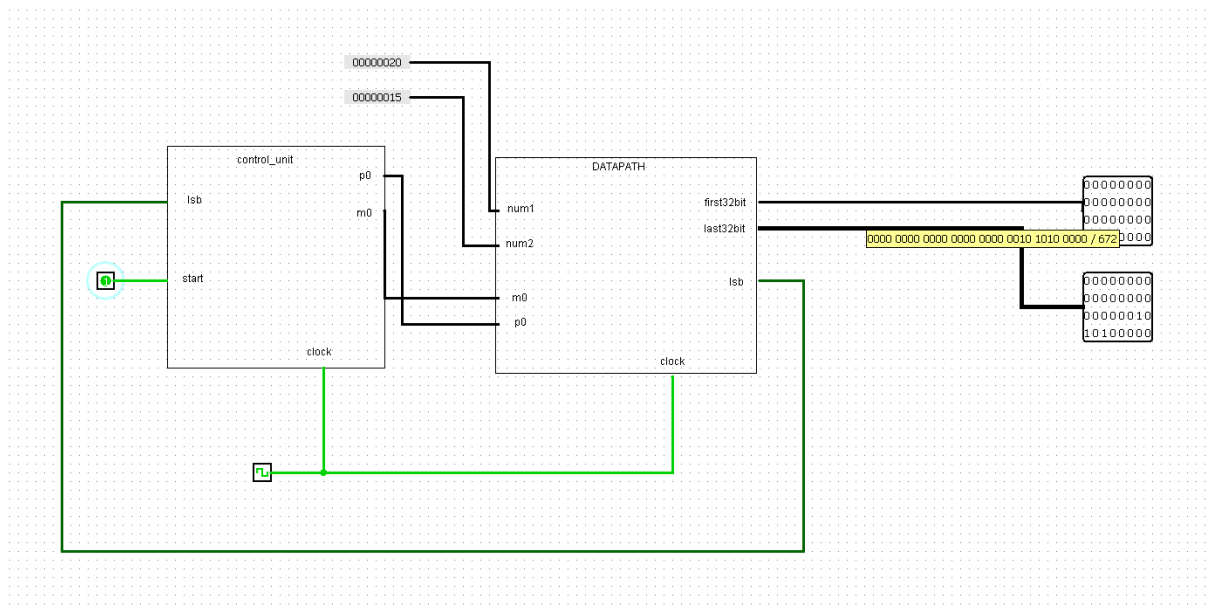


It shows us $21 * 32 = 672$

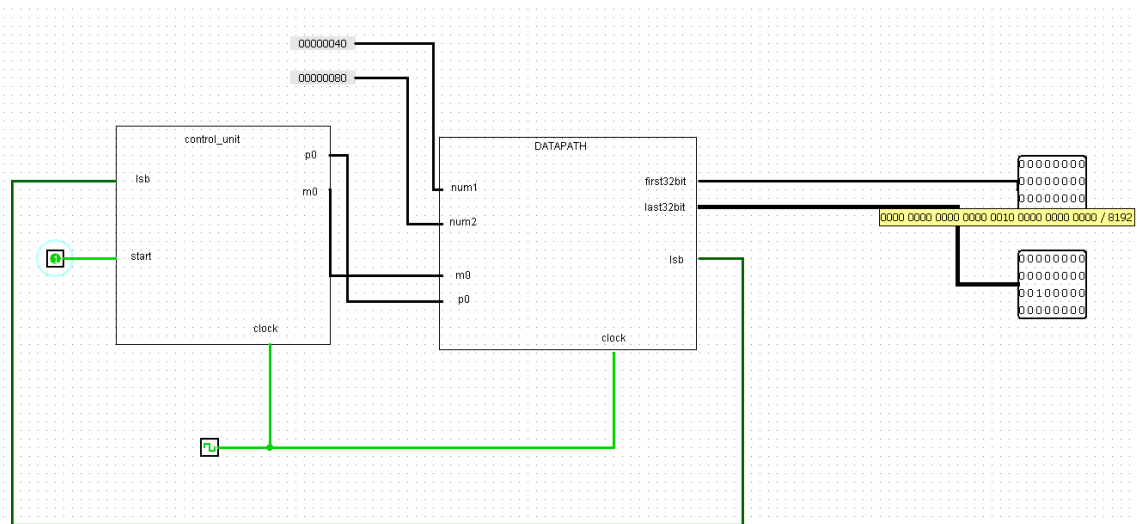

It shows us $128 \times 64 = 8192$

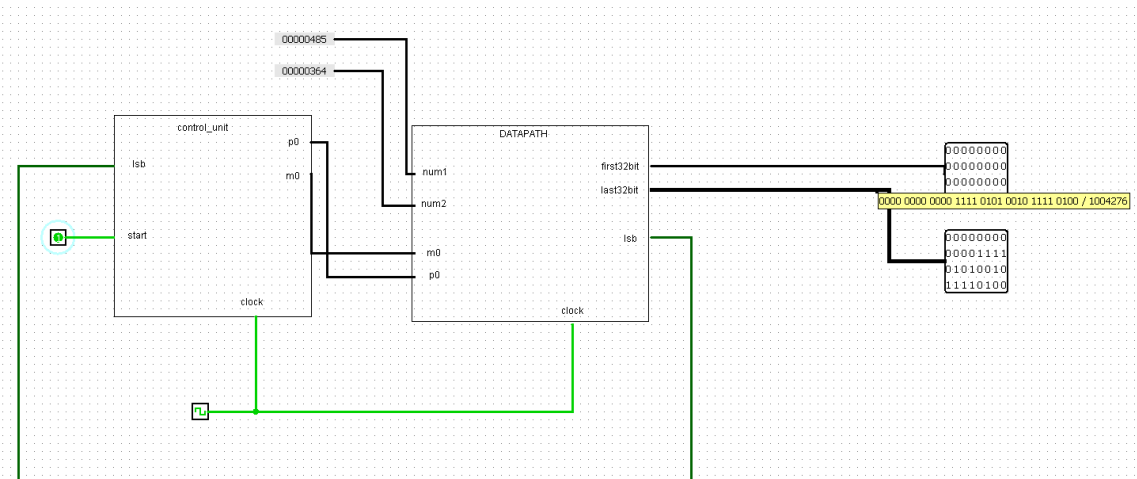

It shows us $1157 \times 868 = 1004276$

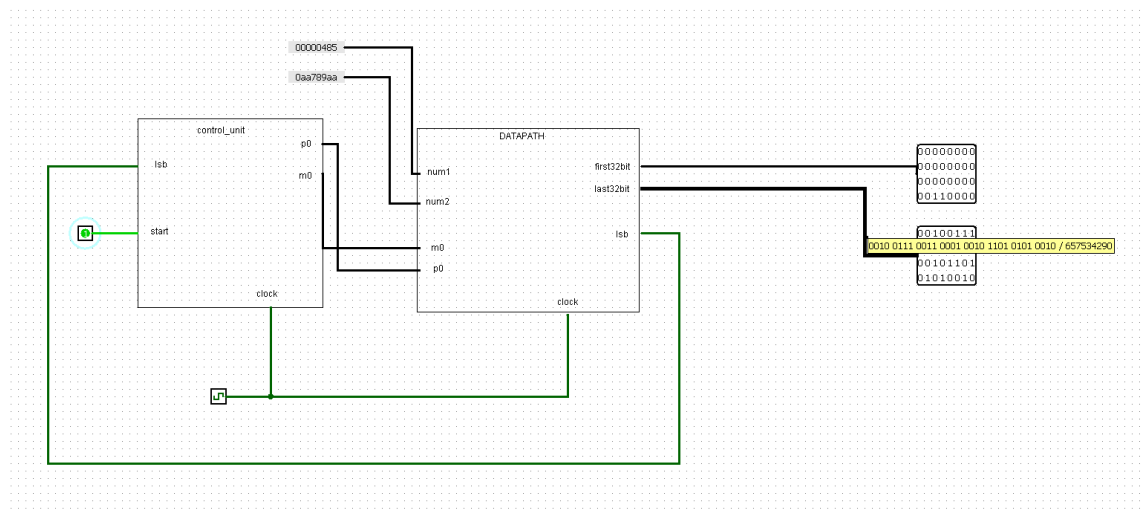

It shows us $178751914 * 1157 = 20815964498$